

1. [30 points] Find v_1 , v_2 , v_3 and i of the circuit in Fig.1 using nodal analysis

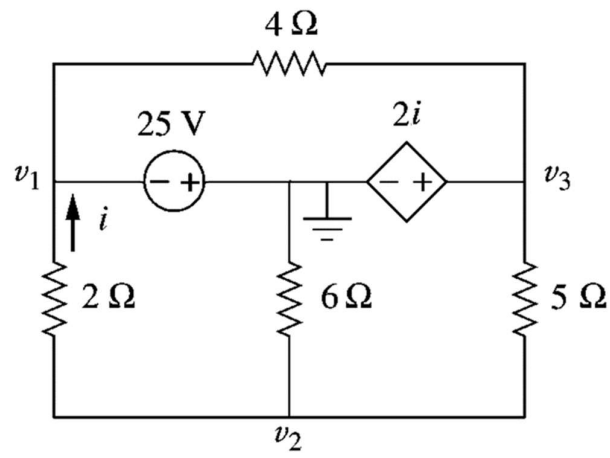


Fig.1

2. [30 points] Find v_o of the circuit in Fig.2 using mesh analysis

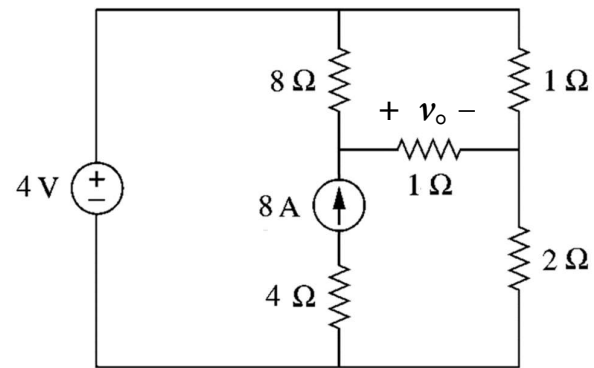


Fig.2

3. [30 points] Find i of the circuit in Fig.3 using superposition

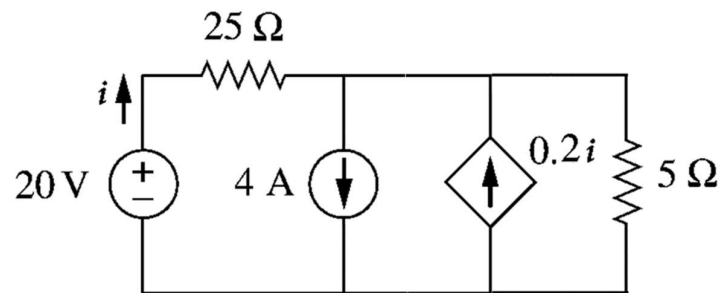


Fig.3

4. [30 points] Find Thevenin's equivalent of the circuit in Fig.4

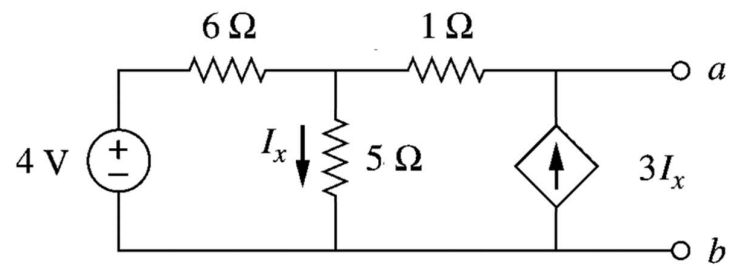


Fig.4

4. [30 points] Find Thevenin's equivalent of the circuit in Fig.4

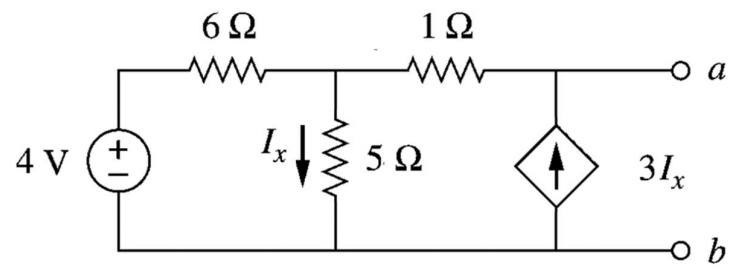


Fig.4

5. [30 points] Find amount of power supplied or absorbed by each element of the circuit.
Specify for each element whether it is supplying or absorbing power.

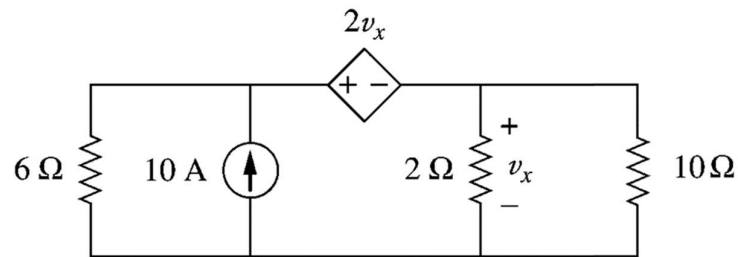


Fig.5

6. [30 points]

6.1 According to the Fig.6 and component list below **draw a schematic diagram** of the circuit.

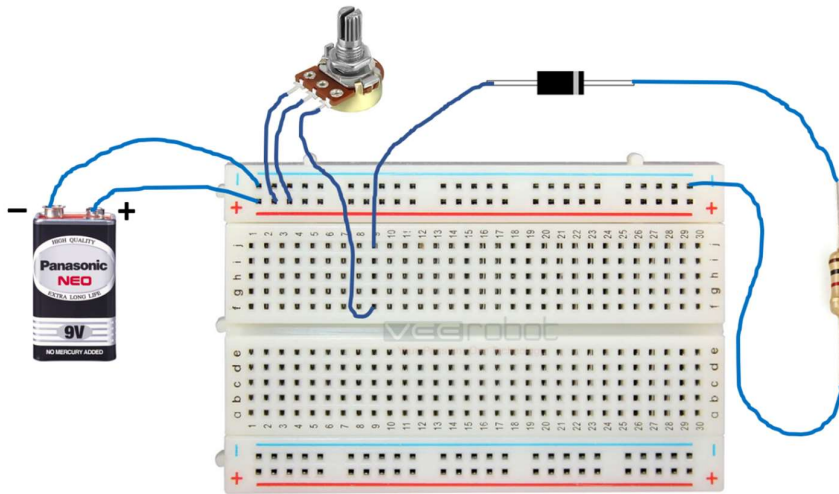


Fig.6

Resistor $1k\ \Omega$ $1/4\ W$ Diode 1N4001 $V_F = 0.7\ V$ Potentiometer $B10k\ \Omega$ Battery $9\ V$.

The complete answer must:

- Use the **correct symbol** for each component
- Write down the **value** of each component next to its symbol
- Write down the **direction of current** flowing in the circuit and **polarities of the voltage** across each component

6.2. Determine the following parameters and their units of each waveform shown in Fig.7.

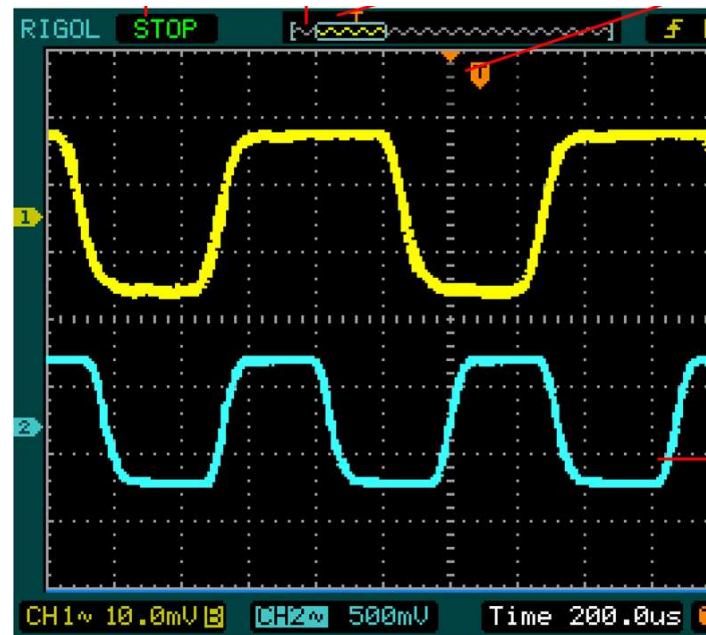


Fig.7

- 1) Amplitude
- 2) Period
- 3) Frequency
- 4) Offset voltage

Clearly show how you calculate. The answer without explanation have no credit.