

Name: Napat Sappasunt Student ID: 65011381 Sent by 30/1/2023

The table beside is the truth table for 2-bit addition.

The inputs are the augend, $A_1 A_0$, and the addend, $B_1 B_0$.

The outputs are the sum $S_1 S_0$ and the carry C_1

Get the remainder of the quotients of the last number in your student ID and 3. Use it to define the outputs Y_1, Y_2 and Y_3 for doing homework. For example, if remainder = 2, then $Y_1 = S_0, Y_2 = C_0$ and $Y_3 = S_1$.

Output Remainder	Y_1	Y_2	Y_3
0	C_1	S_1	S_0
1	S_1	S_0	C_1
2	S_0	C_1	S_1

R1

INPUTS				OUTPUTS		
A_1	A_0	B_1	B_0	C_1	S_1	S_0
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	0	0	1	0
0	0	1	1	0	1	1
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	0	1	1
0	1	1	1	1	0	0
1	0	0	0	0	1	0
1	0	0	1	0	1	1
1	0	1	0	1	0	0
1	0	1	1	1	0	1
1	1	0	0	0	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	1
1	1	1	1	1	1	0

1) Use the Boolean Algebra to simplify the equation for

$$Y_1 = S_1$$

$$\bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 B_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 B_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0 + \bar{A}_1 \bar{A}_0 \bar{B}_1 \bar{B}_0$$

$$\bar{A}_1 \bar{A}_0 \bar{B}_1 + \bar{A}_1 \bar{A}_0 \bar{B}_1 + \bar{A}_1 \bar{A}_0 \bar{B}_1 + \bar{A}_1 \bar{A}_0 \bar{B}_1 + \bar{A}_1 \bar{A}_0 \bar{B}_1 + \bar{A}_1 \bar{A}_0 \bar{B}_1 + \bar{A}_1 \bar{A}_0 \bar{B}_1 + \bar{A}_1 \bar{A}_0 \bar{B}_1$$

$$\bar{A}_0 \bar{B}_1 + A_0$$

2) Use the Karnaugh's Map to minimize the Y_2 and Y_3 .

S_0

$A_1 A_0 \backslash B_1 B_0$	$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
$\bar{A}_1 \bar{A}_0$	0	1	1	0
$\bar{A}_1 A_0$	1	0	0	1
$A_1 \bar{A}_0$	1	0	0	1
$A_1 A_0$	0	1	1	0

$$Y_2 = \bar{B}_1 \bar{B}_0 A_0 + B_1 \bar{B}_0 A_0 + \bar{A}_1 \bar{A}_0 B_0 + A_1 \bar{A}_0 B_0$$

C_1

$A_1 A_0 \backslash B_1 B_0$	$\bar{B}_1 \bar{B}_0$	$\bar{B}_1 B_0$	$B_1 \bar{B}_0$	$B_1 B_0$
$\bar{A}_1 \bar{A}_0$	0	0	0	0
$\bar{A}_1 A_0$	0	0	1	0
$A_1 \bar{A}_0$	0	1	1	1
$A_1 A_0$	0	0	1	1

$$Y_3 = A_1 A_0 B_0 + B_1 B_0 A_0 + A_1 B_1$$